
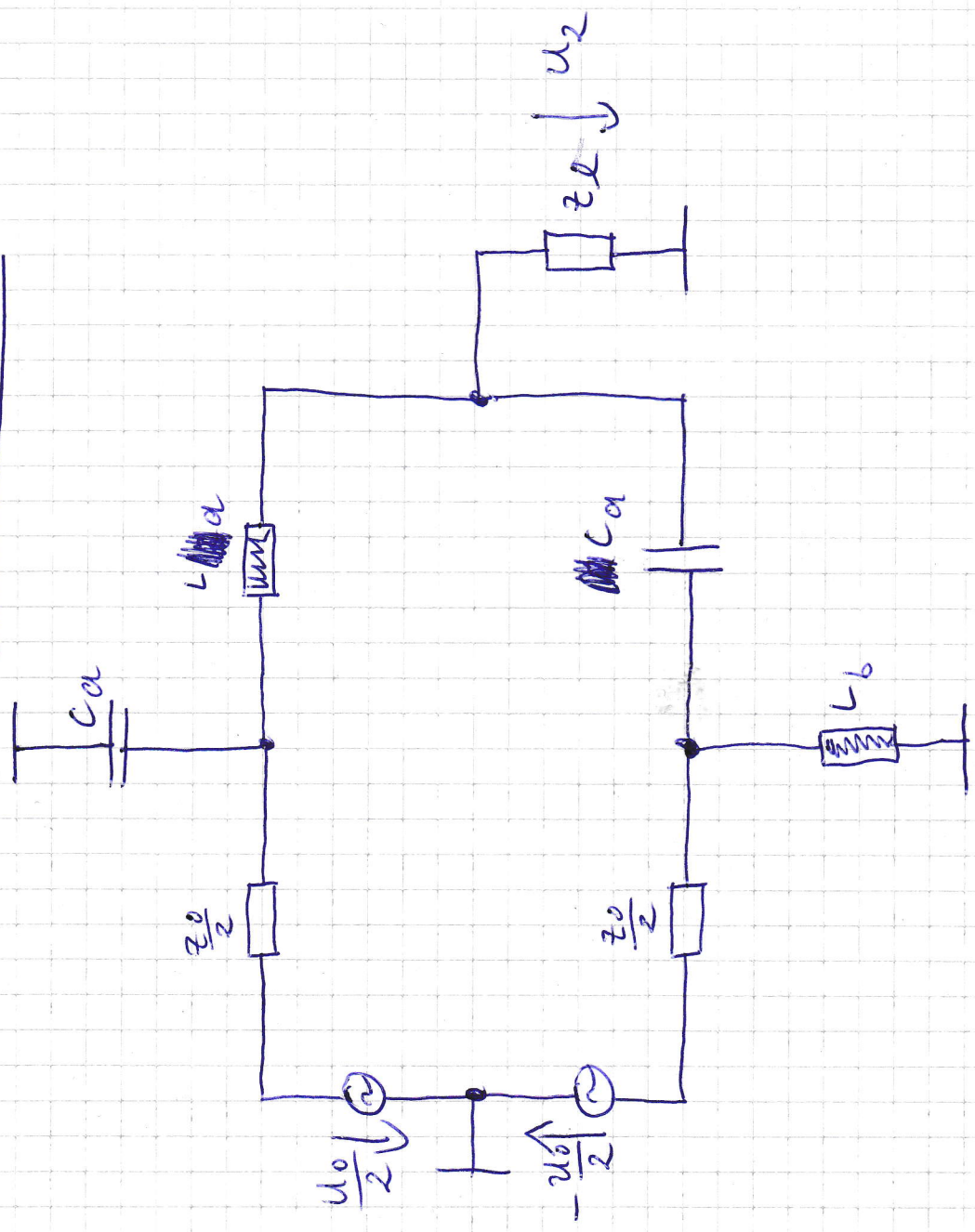


Balun

monofrequent

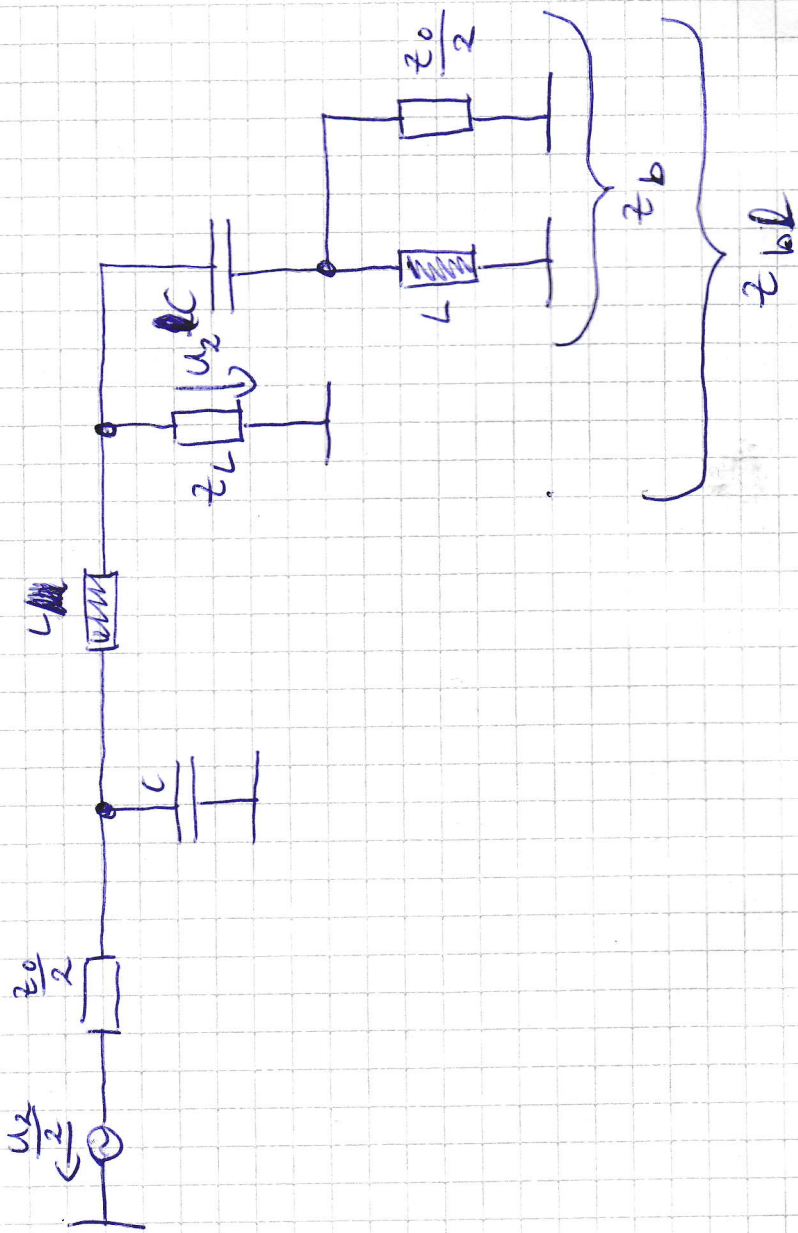

oberer zweig




$$z_b = \frac{1}{j\omega C} + \frac{1}{\frac{1}{j\omega L} + \frac{2}{z_0}}$$

$$z_{bl} = \frac{1}{\frac{1}{z_L} + \frac{1}{z_b}}$$

$$\textcircled{1} \frac{u_2}{u_0} = \frac{\frac{1}{2} z_{bl}}{\frac{1}{z_{bl} + j\omega L} + \frac{z_0}{2}}$$

unterer Zweig

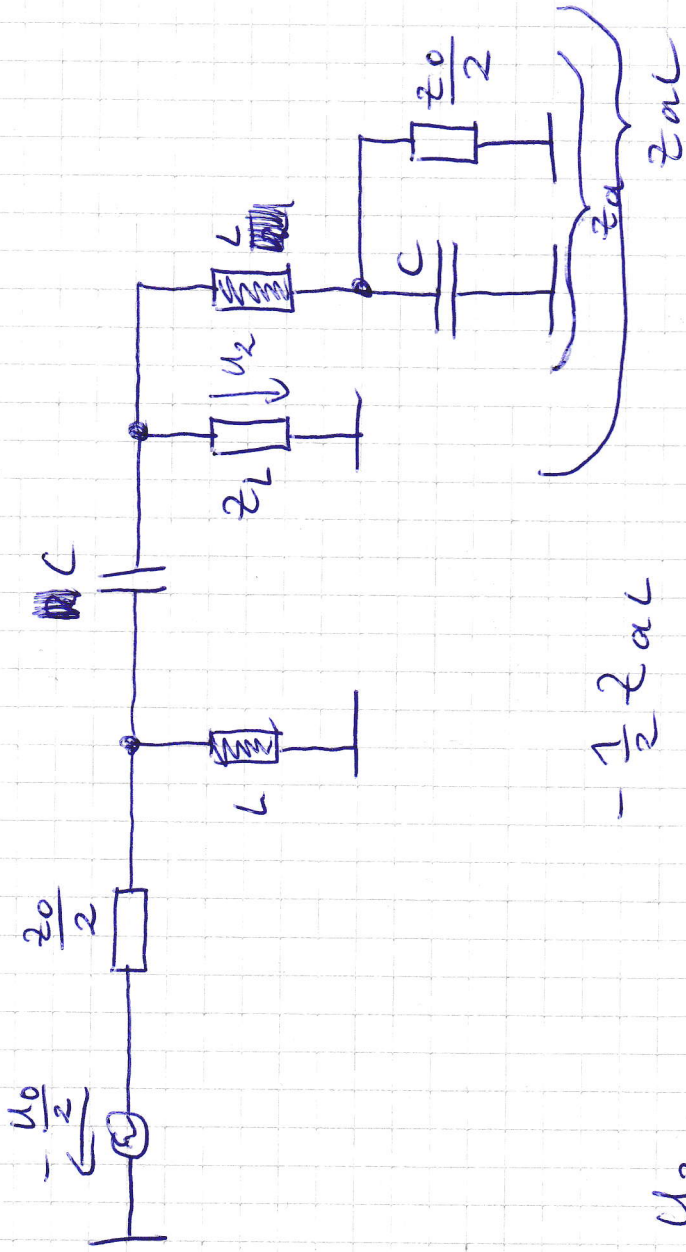

$$z_a = j\omega L + \frac{1}{j\omega C + \frac{2}{z_0}}$$

$$z_{aL} = \frac{1}{\frac{1}{z_L} + \frac{1}{z_a}}$$


$$-\frac{1}{2} z_{aL}$$

$$\textcircled{2} \frac{U_2}{U_0} = \frac{1}{1 + \frac{1}{z_{aL} + \frac{1}{j\omega C}} + \frac{z_0}{2}}$$


$$\frac{U_2}{U_0} = \frac{U_2}{U_0} \textcircled{2}$$

$$Z_{out} = \frac{1}{\frac{1}{Z_a} + \frac{1}{Z_b}}$$

Eingangsimpedanz

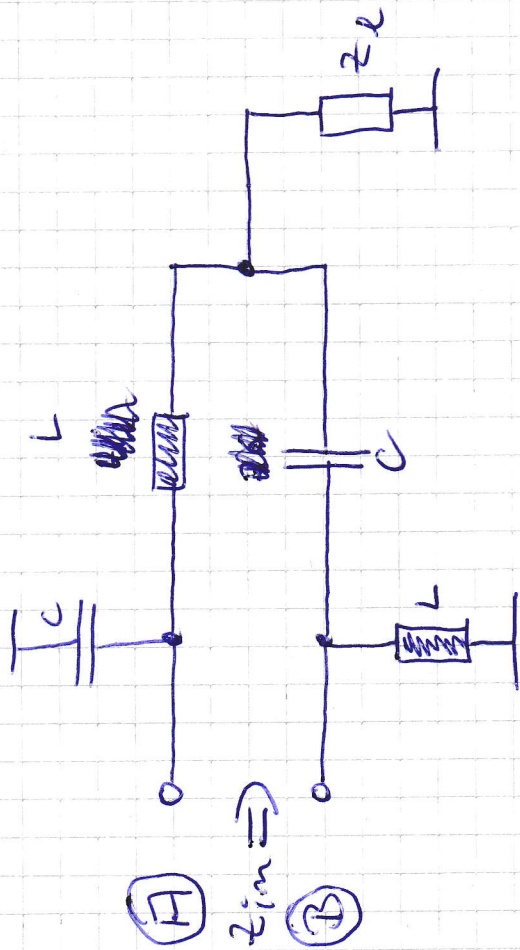

Bückensaltung
 siehe Wikipedia

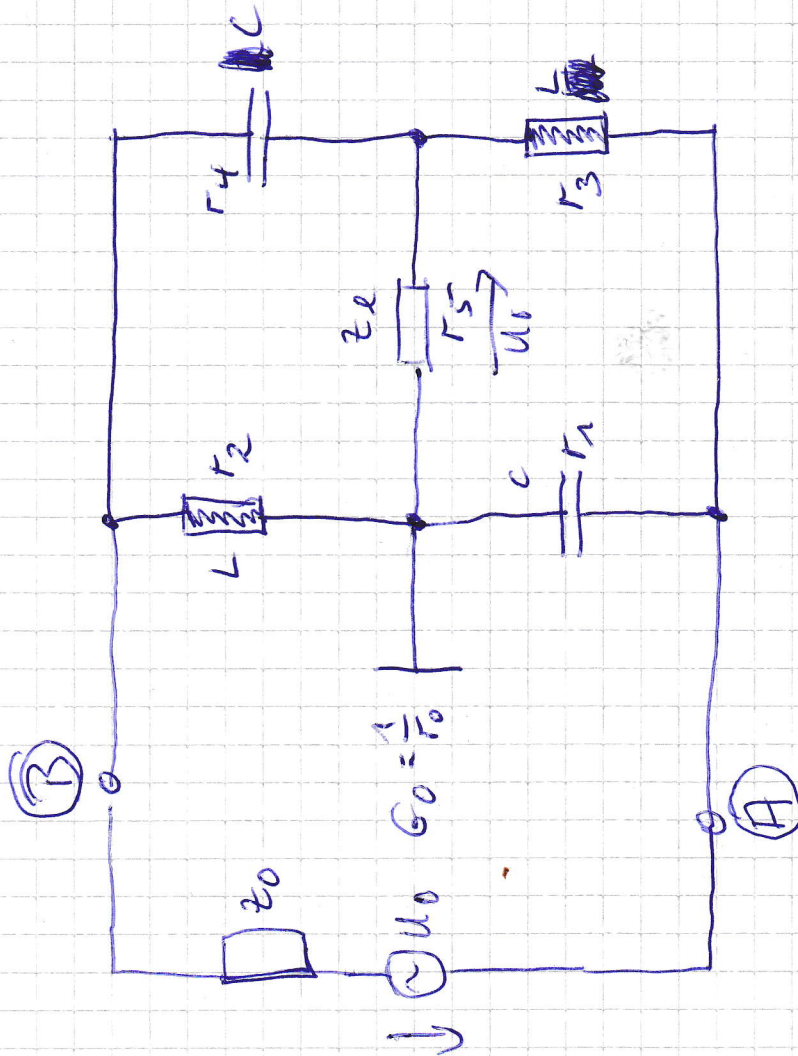

$$d_n = r_5 (r_1 + r_2) (r_3 + r_4) + r_1 r_2 (r_3 + r_4) + (r_1 + r_2) r_3 r_4$$

$$r_0 = \frac{d_n}{(r_5 (r_1 + r_2 + r_3 + r_4) + (r_1 + r_2) (r_3 + r_4))}$$

~~$$u_2 = \frac{r_2 (r_3 + r_4 + r_1 (r_2 + r_3 + r_4))}{r_1 r_2 + r_3 r_4 + (r_1 + r_2) (r_3 + r_4)}$$~~

$$r_1 = r_4, r_2 = r_3$$